



INVERTING AMPLIFIER

Peta Divya Sai

2024081216

M.Tech VLSI Design

Contents

1 Abstract	3
2 Introduction:	4
3 Applications:	4
4 State of the Art	5
5 Design Requirements:	6
6 Working Principle:	6
7 Software Implementation:	7
8 Transient Analysis	8
9 Hardware Implementation:	9
10 Video Link :	10
11 Conclusion:	10
12 References	10

1. Abstract:

An **inverting amplifier** is a fundamental op-amp circuit that amplifies and inverts the input signal, making the output **180° out of phase** with the input. It operates using **negative feedback**, where a portion of the output is fed back to the inverting input to control gain and stability. The voltage gain of the circuit is set by the ratio of the **feedback resistor (Rf) to the input resistor (Rin)**, given by $A_v = -R_f / R_{in}$. This amplifier is widely used in **signal processing, instrumentation, and control systems** due to its precision and predictable gain.

2.Introduction:

An **inverting amplifier** is a fundamental op-amp circuit that amplifies and inverts the input signal, making the output **180° out of phase** with the input. It operates using **negative feedback**, where a portion of the output is fed back to the inverting input to control gain and stability. The voltage gain of the circuit is set by the ratio of the **feedback resistor (Rf) to the input resistor (Rin)**, given by **$A_v = -R_f/R_{in}$** . This amplifier is widely used in **signal processing, instrumentation, and control systems** due to its precision and predictable gain. It provides **excellent linearity, stability, and noise rejection**, making it ideal for filtering and conditioning weak signals. The circuit requires a **dual or single power supply** based on the application needs. Despite its advantages, the inverting amplifier has a **low input impedance**, which may require buffering in some cases. Overall, it is a versatile and essential component in modern analog circuit design.

3.Applications:

Inverting Amplifier circuits are widely used in various fields of electronics.

- **Signal Inversion:** The inverting amplifier is commonly used in **communication and signal processing systems** where phase inversion is required. It ensures that an input voltage of positive polarity is converted into a negative polarity and vice versa. This is crucial in **differential signal processing** and noise cancellation circuits.
- **Audio Signal Processing:** amplifiers play a key role in **audio mixers, equalizers, and active filters**. By adjusting the gain, they help in controlling **volume levels, tone adjustments, and signal balancing** in audio systems. Their ability to provide a stable gain makes them ideal for professional sound equipment.
- **Sensor Signal Conditioning:** Many sensors, such as **thermocouples, strain gauges, and photodiodes**, generate very small voltage or current signals. An inverting amplifier is used to **amplify these weak signals** for further processing. This is widely used in **medical devices, industrial monitoring, and environmental sensing**.
- **Mathematical Operations in Analog Computers:** Inverting amplifiers are essential in **analog computing** for performing operations like **subtraction, integration, and differentiation**. For example, in **integrator circuits**, they are used to generate a time-dependent output based on the input signal, which is useful in **waveform shaping and control systems**.
- **Active Filters:** Inverting amplifiers are used in **low-pass, high-pass, and band-pass filters** to allow or block specific frequency components.

4.State of Art:

Here's a table summarizing the evolution of the **Inverting Amplifier**, including its timeline, price, design advancements, and pros/cons

Era	Technology	Price Range	Design Evolution	Pros	Cons
1940s-1950s	Vacuum Tube Amplifiers	High	Used vacuum tubes for amplification. Bulky and required high power.	High gain, good linearity	Large size, high heat dissipation, expensive
1960s-1970s	Discrete Transistor Op-Amps	Medium	Replaced vacuum tubes with BJTs and FETs in discrete circuits.	Smaller, more efficient, improved stability	Still required multiple components
1970s-1980s	First Integrated Op-Amps (e.g., μ A741)	Low	Introduction of monolithic op-amps (e.g., μ A741), improving reliability and affordability.	Cost-effective, compact, widely used	Limited bandwidth, moderate noise levels
1990s-2000s	High-Speed & Low-Power Op-Amps	Low to Medium	Advanced CMOS & BiCMOS technologies for higher speed and lower power consumption.	Improved bandwidth, lower power consumption	Trade-offs in power vs. speed

5.Design Requirement:

Operational Amplifier (Op-Amp) :Examples: $\mu A741$, LM358, TL081, OP07.

Resistor:Input resistor (R_{in}) and Feedback resistor (R_f) to set gain ($A_v = -R_f/R_{in}$)


Power Supply : Dual supply ($\pm 5V$, $\pm 12V$, or $\pm 15V$) or single supply (e.g., 5V, 9V).

Component	Component Value	Quantity
Resistor	1k	2
Opamp	LM741	1

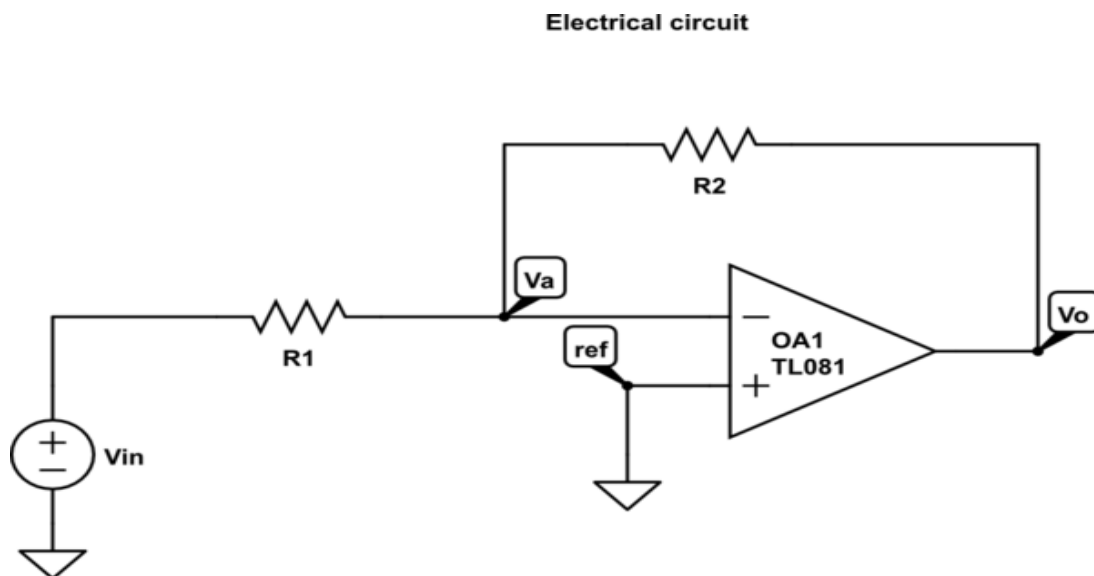6.Working Principle:

The **inverting amplifier** works based on the principle of **negative feedback** and the **virtual ground concept** in an **operational amplifier (op-amp) circuit**. The input signal is applied to the **inverting terminal (-)** through a resistor, while the **non-inverting terminal (+) is grounded**. Due to negative feedback, the inverting terminal maintains a virtual ground, meaning its voltage stays at approximately 0V.


The input current flows through the input resistor and the feedback resistor, as almost no current enters the op-amp itself. According to **Kirchhoff's Current Law (KCL)**, the current entering the inverting terminal must equal the current through the feedback resistor, resulting in an output voltage that is an **inverted and amplified** version of the input. The gain of the amplifier is determined by the ratio of the feedback resistor to the input resistor, given by




$$v_{out} = -(R_f/R_{in})V_{in}$$

The negative sign indicates that the output signal is 180° out of phase with the input. Circuit is widely used in signal processing, filtering, and voltage inversion application.



7. Software Implementation:

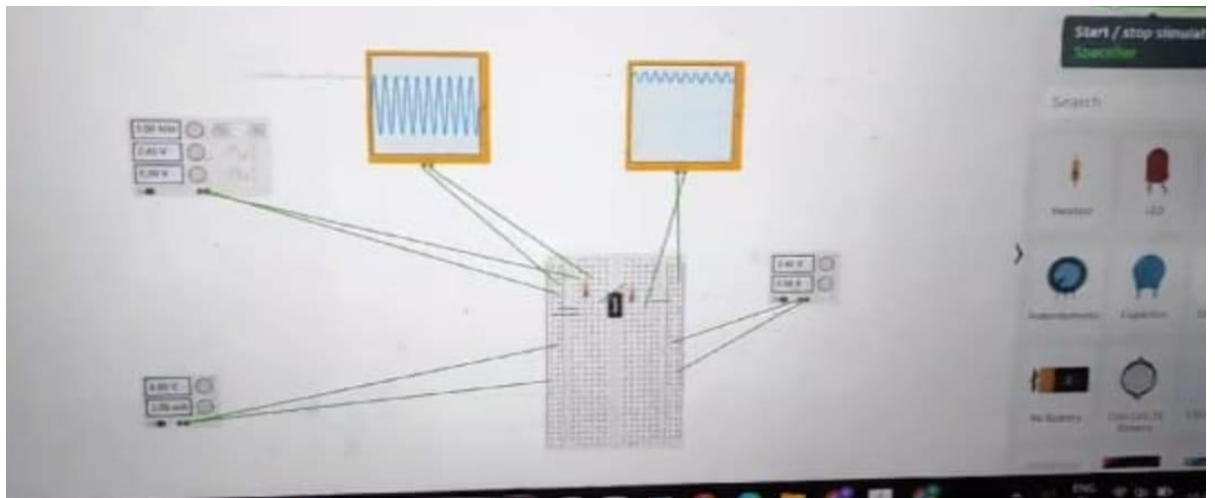

8 . Transient Analysis:

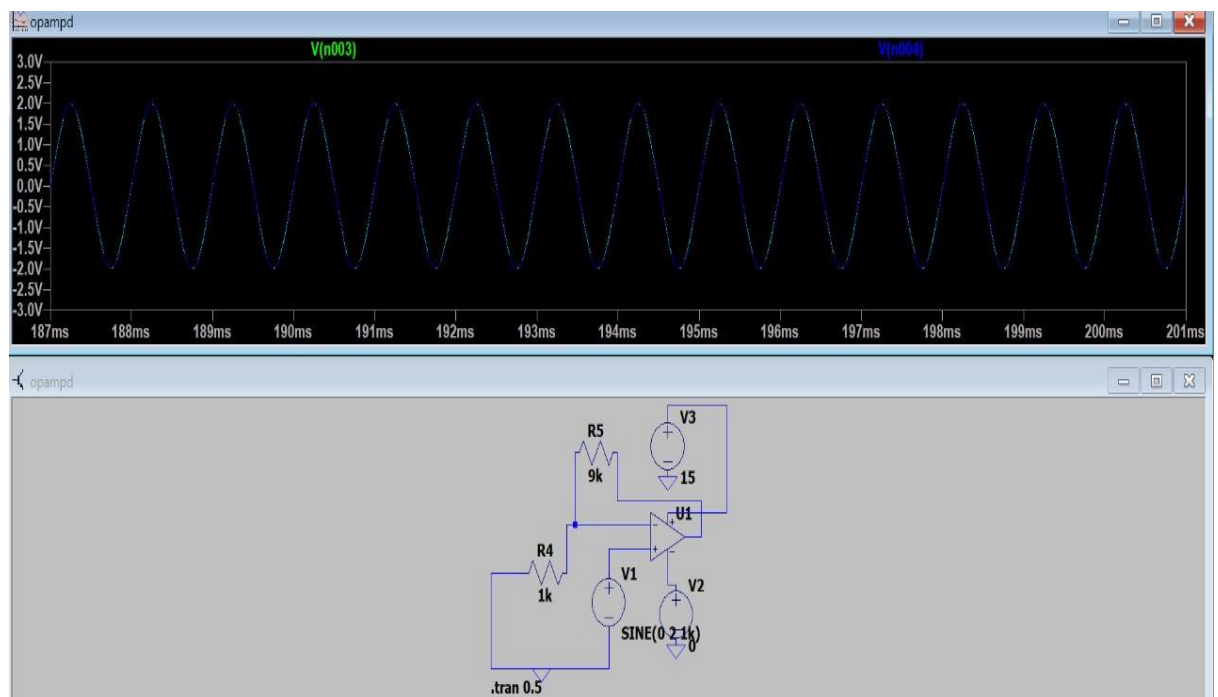

9. Hardware Implementation:

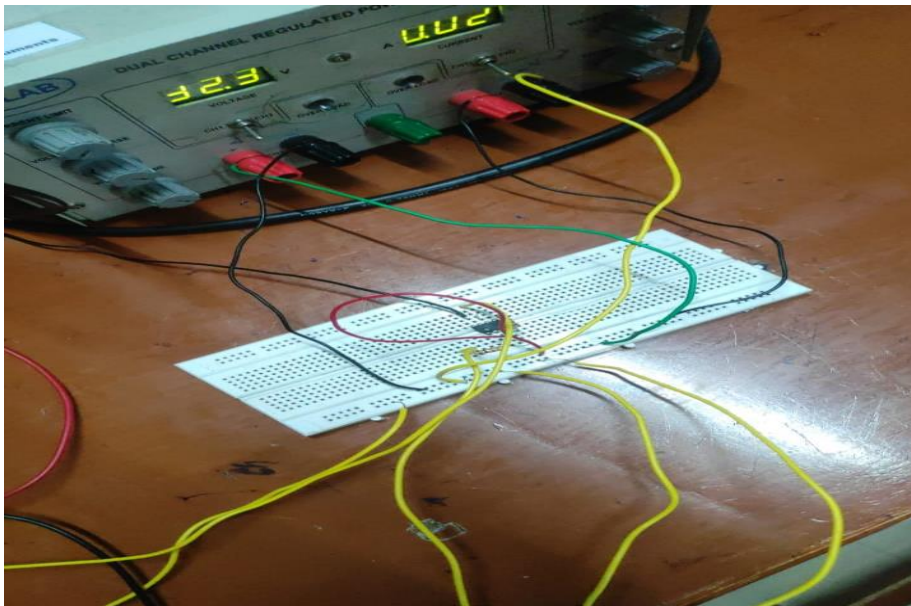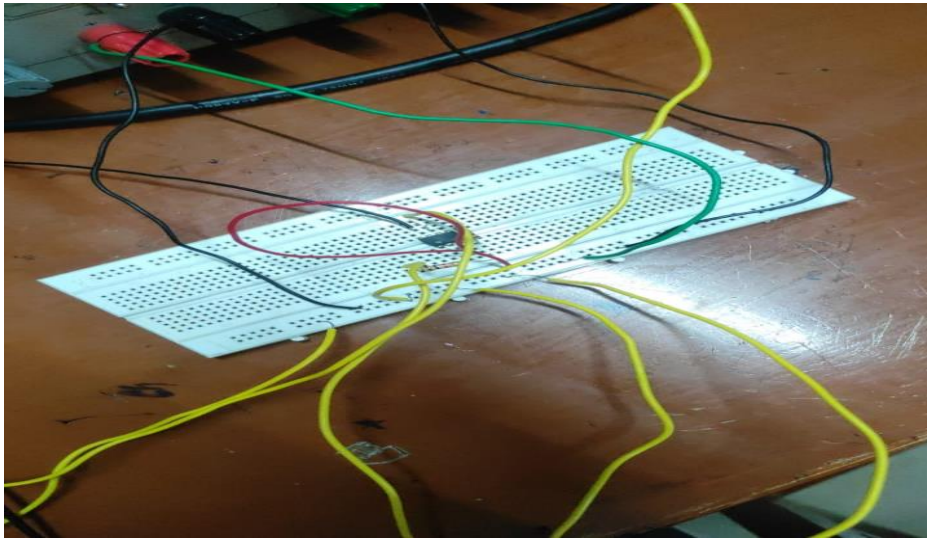

10. Video:

The drive link

11. Conclusion:

The **inverting amplifier** is a crucial circuit in analog electronics, widely used for **signal inversion, amplification, and mathematical operations** in various applications. It operates with **negative feedback**, ensuring high **stability, accuracy, and predictable gain** ($A_v = -R_f/R_{in}$). Due to its **high linearity and low distortion**, it is commonly used in **audio processing, instrumentation, sensor signal conditioning, and active filters**. While it provides excellent **gain control and impedance characteristics**, it has limitations like **low input impedance**, which may require buffering. Advances in **low-noise, high-speed, and precision op-amps** continue to enhance its performance. Overall, the inverting amplifier remains an essential component in modern **electronic, industrial, and communication systems**.

12.References:

- Sedra, A. S., & Smith, K. C. (2016). *Microelectronic Circuits* (7th ed.). Oxford University Press.
- Horowitz, P., & Hill, W. (2015). *The Art of Electronics* (3rd ed.). Cambridge University Press.
- Franco, S. (2014). *Design with Operational Amplifiers and Analog Integrated Circuits* (4th ed.). McGraw-Hill.
- National Semiconductor. (2000). *Op Amp Applications Handbook*. Analog Devices.
- Texas Instruments. (2020). *Operational Amplifiers (Op Amps) Overview and Design Guide*.